


Control Systems

K.SRIHAAS
EE19BTECH11019

SEPTEMBER 7,2020


Find the transfer function, $G(s) = V_0(s)/V_i(s)$, for each operational amplifier circuit shown below

Circuit 1

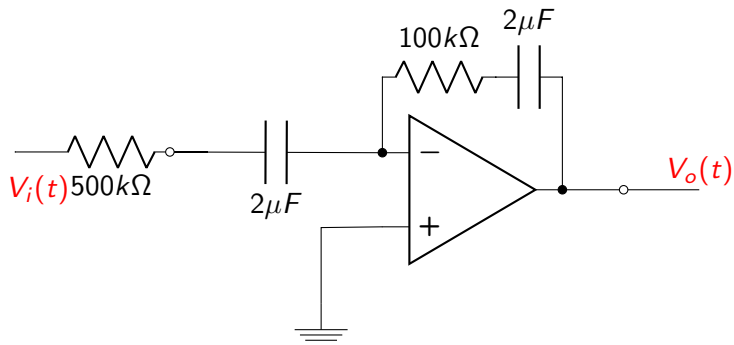

Frequency Domain

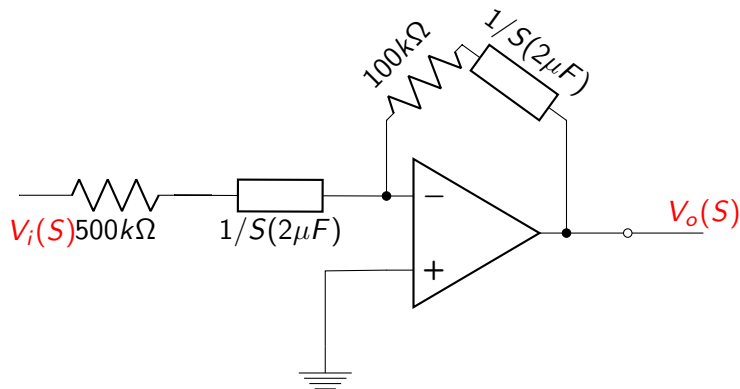Redrawing the Circuit in Frequency Domain



Here we have two Impedance

$$1) Z_2(S) = 100\text{k}\Omega + \frac{1}{S(2\mu\text{F})} = 10^5 + \frac{1}{2 \times 10^{-6}S} = 10^5 \frac{S + 5}{S}$$

$$2) Z_1(S) = 500\text{k}\Omega + \frac{1}{S(2\mu\text{F})} = 5 \times 10^5 + \frac{1}{2 \times 10^{-6}S} = 10^6 \frac{S + 1}{2S}$$

For an inverting Operational Amplifier,


FORMULA:

$$\frac{V_o(S)}{V_i(S)} = -\frac{Z_2(S)}{Z_1(S)}$$


Therefore,

$$\frac{V_o(S)}{V_i(S)} = -\frac{S + 5}{5S + 5}$$

Circuit 2

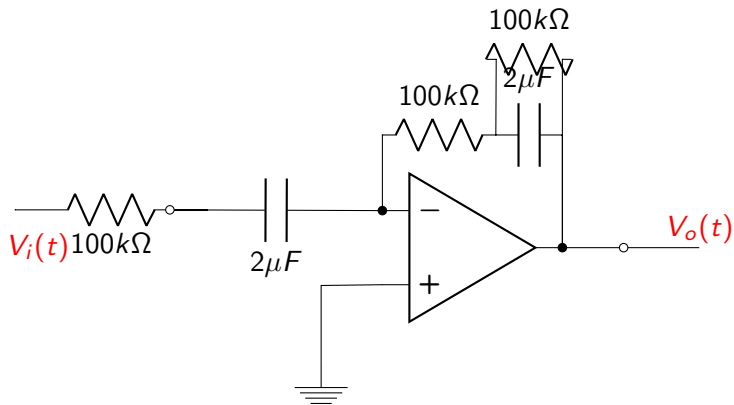

Frequency Domain

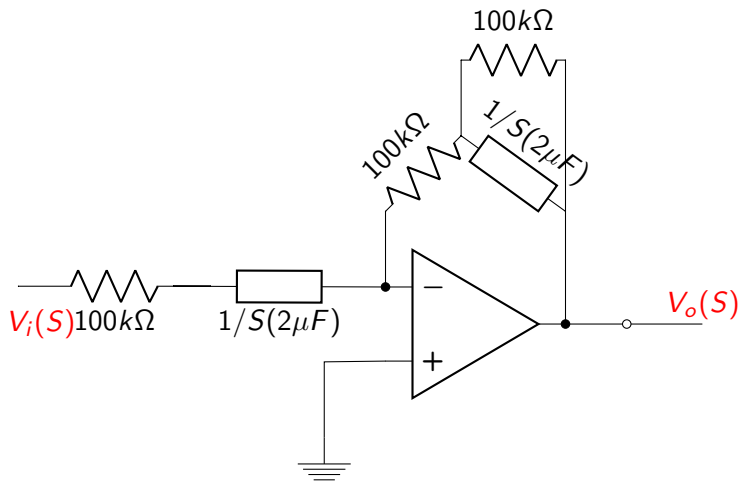

Here we have two Impedance

$$1) Z_2(S) = 100k\Omega + \frac{100k\Omega \times \frac{1}{S(2\mu F)}}{100k\Omega + \frac{1}{S(2\mu F)}} = 10^5 \frac{S + 10}{S + 5}$$

$$2) Z_1(S) = 100k\Omega + \frac{1}{S(2\mu F)} = 10^5 \frac{S + 5}{S}$$

For an inverting Operational Amplifier,

FORMULA:

$$\frac{V_o(S)}{V_i(S)} = -\frac{Z_2(S)}{Z_1(S)}$$

Therefore,

$$\frac{V_o(S)}{V_i(S)} = -\frac{S(S + 10)}{(S + 5)^2}$$